

# 实验报告

2021 年 6 月 9 日

成绩: \_\_\_\_\_

姓名	刘合	学号		班级	
专业	计算机科学与技术		课程名称	计算机组成原理课程设计	
任课老师	冯建文	指导老师		机位号	
实验序号	6	实验名称	取指令及指令译码实验		
实验时间	2021.6.9	实验地点		实验设备号	

## 一、实验目的与要求

### 1、实验目的:

1. 掌握指令存储器、PC 与 IR 的设计方法;
2. 掌握 CPU 取指令操作与指令译码的方法和过程, 掌握指令译码器的设计方法;
3. 理解 RISC-V 立即数的生成与扩展方法, 掌握立即数拼接与扩展器的设计。

### 2、实验要求:

1. 用实验 5 的 acc.s 或 move.s 的机器指令代码, 构造一个 acc.coe 或 move.coe 文件。
2. 使用 Vivado 或者 ISE 的 MemoryIP 核, 新建一个 64X32 位只读存储器作为指令存储器 IM, 并关联 acc.coe 或 move.coe 文件, 初始化其内容。
3. 构造 PC 和 IR 寄存器, 并与上述指令存储器 IM 连接, 构成取指令模块, 如图 11.52 所示
4. 对取指令 模块进行仿真, 确保能正确取出指令, 并且 PC 自增。
5. 编写指令译码模块 IDI, 包括立即数拼接与扩展器模块 ImmU。
6. 对 ImmU 模块进行仿真, 确保立即数拼接与扩展正确。
7. 连接取指令模块和指令译码模块 IDI, 如图所示。
8. 针对使用的实验板卡, 设计取指令与指令译码模块的板级验证实验方案, 编写项层测试模块。表 11.12 给出了本实验 FPGA 引脚信号配置的一个建议, 需要 32 位显示灯, 不一定适合所有的板卡。

表11.12 实验6 信号配置表

	信号名称	配置设备管脚
--	------	--------

输入	PC_Write	逻辑开关
	IR_Write	逻辑开关
时钟	rst_n	按键
	clk_im	按键
输出	imm32[31:0]	8 个数码管
	rs1[4:0]	5 个 LED 灯
	rs2[4:0]	5 个 LED 灯
	rd[4:0]	5 个 LED 灯
	opcode[6:0]	7 个 LED 灯
	funct3[2:0]	3 个 LED 灯
	funct7[6:0]	7 个 LED 灯

图 11.56 给出了另一种板级验证方案，为便于观察，将 PC 和 IR 的内容从顶层模块的端口输出，和生成的立即数一起送到数码管显示，由两位开关进行三选一选择输出；将解析出的各字段，送到显示灯输出。请参考实验 2 中的板级验证设计方法，根据板卡资源自行修改设计。

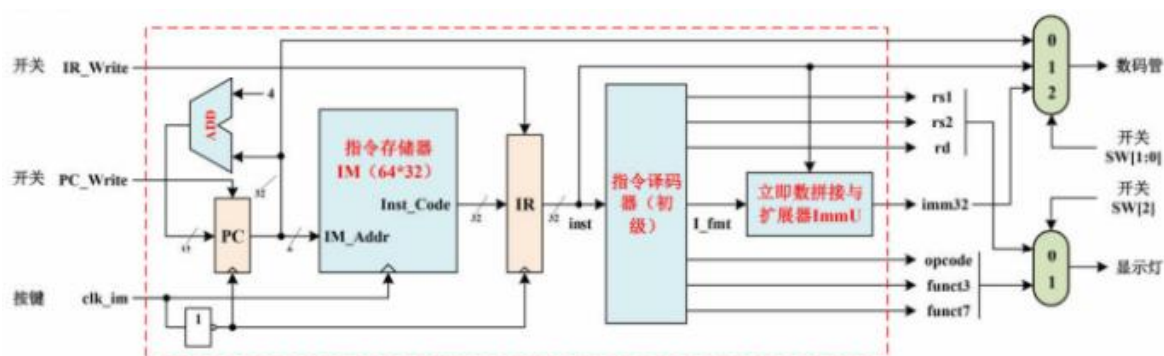


图11.56 实验6的顶层测试模块范例

9. 复位后，按 clk\_im 按键，执行取指令操作，验证读出的指令代码是否和 COE 文件一致，生成的立即数是否正确，解析的各字段是否正确，将实验结果记录到表中。

10. 撰写实验报告，格式见附录，重点内容包括：对仿真结果进行分析；描述你设计的板级验证实验方案、模块结构与连接；说明你的板级操作过程；分析记录下来的板级实验结果、得到有效结论。请力所能及回答或实践本实验的“思考与探索”部分。

### 3. 实验步骤

1. 新建一个 acc.coe 或 move.coe 文件，然后打开实验 5 的 acc.s 或 move.s 汇编语言程序的反汇编文件，将其中的 32 位机器指令代码逐个拷贝到 .coe 文件中，作为指令存储器的初始化数据。

2. 新建一个工程, 通过 IP 核生成向导创建一个 64X32 位的单端口 ROM 存储器, 步骤同实验 4, 但是 Memory Type 选择 Single Port ROM 类型即可; 初始化文件选择前述编辑的 acc .coe 或 move.coe。

3. 编写 PC 寄存器模块和 IR 寄存器模块: 复位时清零; 打入脉冲来临时, 如果写信号有效则执行打入操作。

4. 生成 ROM 存储器的实例作为指令存储器 IM 模块, 并与上述 PC 和 IR 模块连接, 构成取指令模块 IM\_ IF, 如图 11.52 所示。

5. 编写测试代码, 对取指令模块进行仿真, 清零后, 从 0 号单元开始顺序取指令: 当 PC\_ Write 和 IR\_ Write 保持为 1 时, 每来一个 clk\_im, 就从 inst 输出一条指令, 并且 PC+4。

6. 按照图 11.54 以及范例, 编写立即数拼接与扩展器模块 ImmU, 它是组合逻辑电路。

7. 编写测试代码, 对 ImmU 模块进行仿真, 确保立即数拼接与扩展正确。

8. 编写指令译码模块 IDI (如图 11.53), 对指令格式进行译码, 并调用立即数拼接与扩展器模块 ImmU。

9. 如图 11.55 所示, 构造取指令与译码模块 IM\_ IF\_ ID, 调用取指令模块和指令译码模块, 并连接它们。

10. 依据表 11.12 和图 11.56 的提示, 以及实际板卡情况, 设计取指令与译码模块 IM\_ IF\_ ID 的板级验证实验方案, 然后据此编写一个顶层测试模块。

11. 新建管脚约束文件, 进行相应的引脚配置。

12. 生成\*.bit 文件, 下载到实验设备的 FPGA 芯片中。

13. 板级实验: 按照你所设计的实验方案, 操作输入设备、观察输出设备, 预期的验证操作如下:

(1) 按 rst\_n 按键, 将 PC 和 IR 清零, 接下来将从 0 号单元开始取指令;

(2) 拨开关 PC\_ Write=1. IR\_ Write=1, 按动时钟键 clk\_im, 每按一下, 就取出一条指令;

(3) 观察输出设备上读出的指令是否按序读出, 代码是否与初始化的 coe 文件中的指令码一致;

## 二、实验设计与程序代码

## 1、 模块设计说明

程序包含了 7 个模块一个存储器 IP 核：

- 1.顶层模块：有序调用其他模块的程序；
- 2.取指令模块：从指令存储器中依次取出指令，传输给译码模块
- 3.译码模块：把取出的指令解析输出
- 4.显示灯模块：显示指令译码输出的各个部分数据
- 5.分频器模块：是为了给数码管扫描显示模块分配时钟频率；
- 6.数码管扫描显示模块：是为了把 BCD 码数据以十进制数字显示出来
- 7.数据选择模块：选择不同的值存储到存储器。
8. 存储器 IP 核：存储指令数据

## 2.实验程序源代码及注释等

```
module dingceng(CLR,clk_1M,SW,K,rst_n,IR_Write,PC_Write,clk_im,LED,AN,seg);  
    input CLR;  
    input clk_1M;  
    input [1:0]SW;  
    input K;  
    input rst_n;  
    input IR_Write;  
    input PC_Write;  
    input clk_im;  
    output [16:0]LED;  
    output [7:0]AN,seg;  
    wire [4:0]rs1;  
    wire [4:0]rs2;  
    wire [4:0]rd;  
    wire [6:0]opcode;  
    wire [2:0]funct3;  
    wire [6:0]funct7;  
    wire [31:0]PC,inst,imm32,F;  
    wire CLK;
```

```

zhilin oo(rst_n,IR_Write,PC_Write,clk_im,inst,PC);
yima pp(inst,rs1,rs2,rd,imm32,opcode,funct3,funct7);
threeone qq(SW,PC,inst,imm32,F);
xsd rr(K,rs1,rs2,rd,opcode,funct3,funct7,LED[16:0]);
fpq ss(CLR,clk_1M,CLK);
smgsm tt(CLK,CLR,F,AN,seg);
endmodule

```

```

module zhilin(rst_n,IR_Write,PC_Write,clk_im,inst,PC);
    input rst_n;
    input IR_Write;
    input PC_Write;
    input clk_im;
    output [31:0]inst;
    output [31:0]PC;
    wire clk_fim;
    wire [31:0]PC_Out;
    wire [31:0]Inst_Code;
    assign clk_fim=~clk_im;
    PC aa(rst_n,PC_Write,clk_fim,PC_Out);
    assign PC=PC_Out;
    RAM_B IM(      //存储器
.clka(clk_im),    // input wire clka
.addra(PC_Out[7:2]), // input wire [5 : 0] addra
.douta(Inst_Code) // output wire [31 : 0] douta
);
    IR cc(Inst_Code,clk_fim,IR_Write,inst);
Endmodule

```

```
module PC(rst_n,PC_Write,clk_fim,PC_Out);//程序计数器 PC
```

```
    input rst_n;
```

```
    input PC_Write;
```

```
    input clk_fim;
```

```
    output reg [31:0]PC_Out;
```

```
    initial
```

```
        begin
```

```
            PC_Out<=0;
```

```
        end
```

```
    always@(posedge clk_fim or posedge rst_n)
```

```
    begin
```

```
        if(rst_n==0)
```

```
            PC_Out<=0;
```

```
        else
```

```
            begin
```

```
                if(PC_Write==1)
```

```
                    PC_Out<=PC_Out+4;
```

```
                else
```

```
                    PC_Out<=PC_Out;
```

```
            end
```

```
    end
```

```
endmodule
```

```
module IR(Inst_Code,clk_fim,IR_Write,inst);
```

```
    input [31:0]Inst_Code;
```

```
    input clk_fim;
```

```
    input IR_Write;
```

```
    output reg [31:0]inst;
```

```
    always@(posedge clk_fim)
```

```
    begin
```

```

        if(IR_Write==1)
            inst<=Inst_Code;
        end
    endmodule

```

```

module yima(inst,rs1,rs2,rd,imm32,opcode,funct3,funct7);
    input [31:0]inst;
    output [4:0]rs1;
    output [4:0]rs2;
    output [4:0]rd;
    output [31:0]imm32;
    output [6:0]opcode;
    output [2:0]funct3;
    output [6:0]funct7;
    wire [6:0]I_fmt;
    ID1 dd(inst,rs1,rs2,rd,I_fmt,opcode,funct3,funct7);
    ImmU ee(inst,I_fmt,imm32);
Endmodule

```

```

module ID1(inst,rs1,rs2,rd,I_fmt,opcode,funct3,funct7);
    input [31:0]inst;
    output [4:0]rs1;
    output [4:0]rs2;
    output [4:0]rd;
    output [6:0]I_fmt;
    output [6:0]opcode;
    output [2:0]funct3;
    output [6:0]funct7;
    wire R_Type,I_Type,S_Type,B_Type,U_Type,J_Type,YW_Type;
    assign I_fmt={R_Type,I_Type,S_Type,B_Type,U_Type,J_Type,YW_Type};

```

```

`define OP_R   7'b0110011
assign R_Type=(opcode==`OP_R);
`define OP_I1  7'b0010011
`define OP_I2  7'b0000011
assign I_Type=(opcode==`OP_I1||opcode==`OP_I2);
`define OP_S   7'b0100011
assign S_Type=(opcode==`OP_S);
`define OP_B   7'b1100011
assign B_Type=(opcode==`OP_B);
`define OP_U1  7'b0110111
`define OP_U2  7'b0010111
assign U_Type=(opcode==`OP_U1||opcode==`OP_U2);
`define OP_J   7'b1101111
assign J_Type=(opcode==`OP_J);
`define OP_I3  7'b1100111
assign YW_Type=(opcode==`OP_I3);
assign opcode=inst[6:0];
assign rs1=inst[19:15];
assign rs2=inst[24:20];
assign rd=inst[11:7];
assign funct3=inst[14:12];
assign funct7=inst[31:25];
endmodule

```

```

module ImmU(inst,I_fmt,imm32);
    input [31:0]inst;
    input [6:0]I_fmt;
    output reg [31:0]imm32;
    wire [31:0]I_imm;
    wire [31:0]S_imm;

```



```

wire [31:0]B_imm;
wire [31:0]U_imm;
wire [31:0]J_imm;
wire [31:0]yw_imm;
assign I_imm={ {20{inst[31]}} ,inst[31:20]};
assign S_imm={ {20{inst[31]}} ,inst[31:25],inst[11:7]};
assign B_imm={ {20{inst[31]}} ,inst[7],inst[30:25],inst[11:8],1'b0};
assign U_imm={ inst[31:12],{12{1'b0}}} };
assign J_imm={ {12{inst[31]}} ,inst[19:12],inst[20],inst[30:21],1'b0};
assign yw_imm={ {20{1'b0}} ,inst[11:0]};
always@(*)
begin
    case(I_fmt)
        7'b0100000: imm32=I_imm;//I
        7'b0010000: imm32=S_imm;//S
        7'b0001000: imm32=B_imm;//B
        7'b0000100: imm32=U_imm;//U
        7'b0000010: imm32=J_imm;//J
        7'b0000001:imm32=yw_imm;//I 型移位
        default:imm32=0;
    endcase
end
endmodule

module threeone(SW,PC,inst,imm32,F);//三选一 A,B,F 输出到数码管显示
input [1:0]SW;
input [31:0]PC;
input [31:0]inst;
input [31:0]imm32;
output reg [31:0]F;

```

```

always@(*)
begin
    case(SW)
        2'b00:begin F=PC; end
        2'b01:begin F=inst; end
        2'b10:begin F=imm32; end
        default:begin F=PC; end
    endcase
end
endmodule

module xsd(K,rs1,rs2,rd,opcode,funct3,funct7,LED);
    input K;
    input [4:0]rs1,rs2,rd;
    input [6:0]opcode;
    input [2:0]funct3;
    input [6:0]funct7;
    output reg [16:0]LED;
    always@(*)
    begin
        case(K)
            0: begin
                LED[16:12]=rs1;
                LED[11:7]=rs2;
                LED[6:2]=rd;
                LED[1:0]=2'b00;
            end
            1: begin
                LED[16:10]=opcode;
                LED[9:7]=funct3;

```

```

        LED[6:0]=funct7;
    end
endcase
end
endmodule

```

```

module fpq(CLR,clk_1M,CLK);          //分频器模块
    input CLR;
    input clk_1M;
    output reg CLK;
    reg [8:0]counter;
    always@(negedge CLR or posedge clk_1M)
    begin
        if(!CLR)
            begin
                counter<=9'd0;
                CLK<=1'b0;
            end
        else if(counter==9'd500)
            begin
                CLK<=~CLK;
                counter<=9'd0;
            end
        else
            counter<=counter+1'b1;
        end
    end
endmodule

```

```

module smgsm(CLK,CLR,Choice,AN,seg);//数码管扫描显示模块

```

```

input CLK; //扫描的间隔始终，控制数码管轮流点亮的频率
input CLR; //复位信号，用于初始化状态
input[31:0]Choice;
output reg [7:0]AN;//位选
output reg [7:0]seg; //段选
reg [3:0] data;
reg [2:0] bit_sel; //数码管计数器指示，000~111 最左到最右
always@(negedge CLR or posedge CLK)
begin
    if(!CLR)
        bit_sel<=3'b000;
    else
        bit_sel<=bit_sel+1'b1;
end
always@(*)
begin
    case(bit_sel)
        3'b000:data<=Choice[3:0];
        3'b001:data<=Choice[7:4];
        3'b010:data<=Choice[11:8];
        3'b011:data<=Choice[15:12];
        3'b100:data<=Choice[19:16];
        3'b101:data<=Choice[23:20];
        3'b110:data<=Choice[27:24];
        3'b111:data<=Choice[31:28];
        default:data<=data;
    endcase
end
always@(*)
begin

```

```

        case(bit_sel)
            3'b000:AN=8'b11111110;
            3'b001:AN=8'b11111101;
            3'b010:AN=8'b11111011;
            3'b011:AN=8'b11110111;
            3'b100:AN=8'b11101111;
            3'b101:AN=8'b11011111;
            3'b110:AN=8'b10111111;
            3'b111:AN=8'b01111111;
            default:AN=8'b11111111;
        endcase
    end
always@(*)
begin
    case(data)
        0:seg<=8'b00000011;
        1:seg<=8'b10011111;
        2:seg<=8'b00100101;
        3:seg<=8'b00001101;
        4:seg<=8'b10011001;
        5:seg<=8'b01001001;
        6:seg<=8'b01000001;
        7:seg<=8'b00011111;
        8:seg<=8'b00000001;
        9:seg<=8'b00001001;
        10:seg<=8'b00010001;
        11:seg<=8'b11000001;
        12:seg<=8'b01100011;
        13:seg<=8'b10000101;
        14:seg<=8'b01100001;
    endcase
end

```

```

        15:seg<=8'b01110001;

        default:seg<=8'b11111111;

    endcase

end

endmodule

```

### 三、实验仿真

#### 1、 仿真代码

//下面是取指令模块的仿真激励代码

```

module qzfz();

//INPUT

reg rst_n;
reg IR_Write;
reg PC_Write;
reg clk_im;

//OUTPUT

wire [31:0]inst;

initial
    begin
        rst_n=1;clk_im=0;IR_Write=0;PC_Write=1;
    end

always
    begin
        #200  rst_n=~rst_n;
    end

always
    begin
        #25  clk_im=~clk_im;
    end

always

```

```

        begin
            #40  IR_Write=~IR_Write;
        end
always
    begin
        #30  PC_Write=~PC_Write;
    end

    zhilin ff(rst_n,IR_Write,PC_Write,clk_im,inst);
endmodule

//下面是译码模块的仿真激励代码
module ymfz();
//INPUT
reg [31:0]inst;
//OUTPUT
wire [4:0]rs1;
wire [4:0]rs2;
wire [4:0]rd;
wire [31:0]imm32;
wire [6:0]opcode;
wire [2:0]funct3;
wire [6:0]funct7;
initial
    begin
        inst=32'h0000_02b3;//add  R 型
        #50 inst=32'hfff3_8393;//addi I 型
        #50 inst=32'h09c0_2023;//SW  S 型
    end

    yima kk(inst,rs1,rs2,rd,imm32,opcode,funct3,funct7);
endmodule

RAM_B vv(

```

```

.clka(clka),    // input wire clka
.wea(wea),      // input wire [0 : 0] wea
.addra(addra),  // input wire [5 : 0] addra
.dina(dina),    // input wire [31 : 0] dina
.douta(douta)   // output wire [31 : 0] douta
);


endmodule

```


## 2、仿真波形

（运行仿真时，波形截图）

取指令：

 

译码：

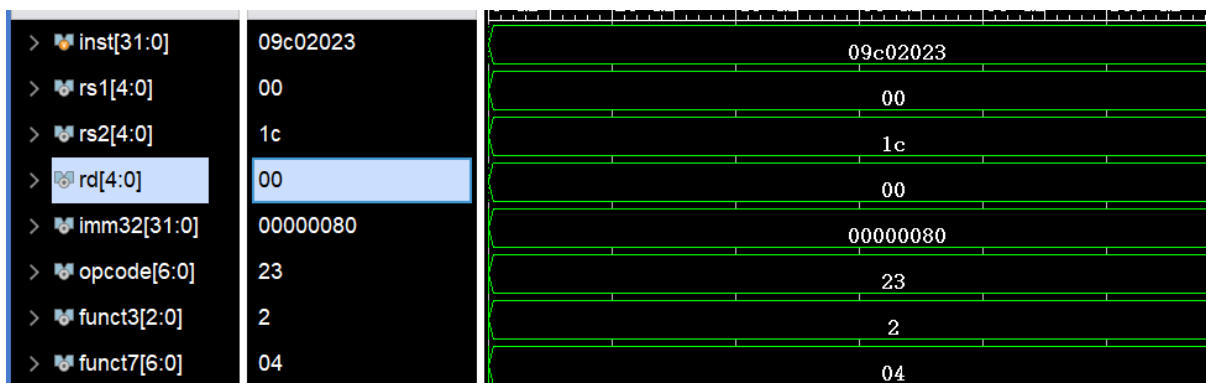


## 3、仿真结果分析

取指令与译码功能都符合预期的效果。逻辑成功。

## 四、电路图



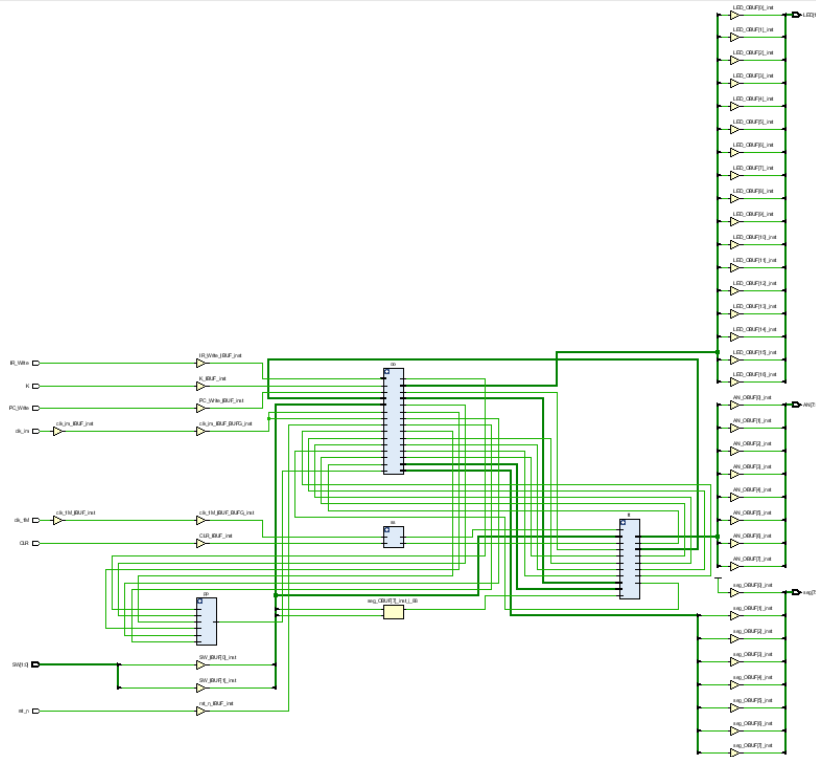

## 五、引脚配置

（引脚约束文件的内容，描述主要配置情况）

```
set_property IOSTANDARD LVCMOS18 [get_ports clk_im]
set_property IOSTANDARD LVCMOS18 [get_ports {AN[7]}]
set_property IOSTANDARD LVCMOS18 [get_ports {AN[6]}]
set_property IOSTANDARD LVCMOS18 [get_ports {AN[5]}]
set_property IOSTANDARD LVCMOS18 [get_ports {AN[4]}]
set_property IOSTANDARD LVCMOS18 [get_ports {AN[3]}]
set_property IOSTANDARD LVCMOS18 [get_ports {AN[2]}]
set_property IOSTANDARD LVCMOS18 [get_ports {AN[1]}]
set_property IOSTANDARD LVCMOS18 [get_ports {AN[0]}]
set_property IOSTANDARD LVCMOS18 [get_ports {LED[16]}]
set_property IOSTANDARD LVCMOS18 [get_ports {LED[15]}]
set_property IOSTANDARD LVCMOS18 [get_ports {LED[14]}]
set_property IOSTANDARD LVCMOS18 [get_ports {LED[13]}]
set_property IOSTANDARD LVCMOS18 [get_ports {LED[12]}]
set_property IOSTANDARD LVCMOS18 [get_ports {LED[11]}]
```

```
set_property IOSTANDARD LVCMOS18 [get_ports {LED[10]}]
set_property IOSTANDARD LVCMOS18 [get_ports {LED[9]}]
set_property IOSTANDARD LVCMOS18 [get_ports {LED[8]}]
set_property IOSTANDARD LVCMOS18 [get_ports {LED[7]}]
set_property IOSTANDARD LVCMOS18 [get_ports {LED[6]}]
set_property IOSTANDARD LVCMOS18 [get_ports {LED[5]}]
set_property IOSTANDARD LVCMOS18 [get_ports {LED[4]}]
set_property IOSTANDARD LVCMOS18 [get_ports {LED[3]}]
set_property IOSTANDARD LVCMOS18 [get_ports {LED[2]}]
set_property IOSTANDARD LVCMOS18 [get_ports {LED[1]}]
set_property IOSTANDARD LVCMOS18 [get_ports {LED[0]}]
set_property IOSTANDARD LVCMOS18 [get_ports {seg[7]}]
set_property IOSTANDARD LVCMOS18 [get_ports {seg[6]}]
set_property IOSTANDARD LVCMOS18 [get_ports {seg[5]}]
set_property IOSTANDARD LVCMOS18 [get_ports {seg[4]}]
set_property IOSTANDARD LVCMOS18 [get_ports {seg[3]}]
set_property IOSTANDARD LVCMOS18 [get_ports {seg[2]}]
set_property IOSTANDARD LVCMOS18 [get_ports {seg[1]}]
set_property IOSTANDARD LVCMOS18 [get_ports {seg[0]}]
set_property IOSTANDARD LVCMOS18 [get_ports {SW[1]}]
set_property IOSTANDARD LVCMOS18 [get_ports {SW[0]}]
set_property IOSTANDARD LVCMOS18 [get_ports clk_1M]
set_property IOSTANDARD LVCMOS18 [get_ports CLR]
set_property IOSTANDARD LVCMOS18 [get_ports IR_Write]
set_property IOSTANDARD LVCMOS18 [get_ports K]
set_property IOSTANDARD LVCMOS18 [get_ports PC_Write]
set_property IOSTANDARD LVCMOS18 [get_ports rst_n]
set_property PACKAGE_PIN E3 [get_ports clk_1M]
set_property PACKAGE_PIN N17 [get_ports CLR]
set_property PACKAGE_PIN U6 [get_ports {LED[16]}]
```

```
set_property PACKAGE_PIN R5 [get_ports {LED[15]}]
set_property PACKAGE_PIN U7 [get_ports {LED[14]}]
set_property PACKAGE_PIN R6 [get_ports {LED[13]}]
set_property PACKAGE_PIN R7 [get_ports {LED[12]}]
set_property PACKAGE_PIN U8 [get_ports {LED[11]}]
set_property PACKAGE_PIN T8 [get_ports {LED[10]}]
set_property PACKAGE_PIN V9 [get_ports {LED[9]}]
set_property PACKAGE_PIN T10 [get_ports {LED[8]}]
set_property PACKAGE_PIN V11 [get_ports {LED[7]}]
set_property PACKAGE_PIN T11 [get_ports {LED[6]}]
set_property PACKAGE_PIN V12 [get_ports {LED[5]}]
set_property PACKAGE_PIN R12 [get_ports {LED[4]}]
set_property PACKAGE_PIN U13 [get_ports {LED[3]}]
set_property PACKAGE_PIN R13 [get_ports {LED[2]}]
set_property PACKAGE_PIN U14 [get_ports {LED[1]}]
set_property PACKAGE_PIN T15 [get_ports {LED[0]}]
set_property PACKAGE_PIN C9 [get_ports {AN[7]}]
set_property PACKAGE_PIN C10 [get_ports {AN[6]}]
set_property PACKAGE_PIN D10 [get_ports {AN[5]}]
set_property PACKAGE_PIN C11 [get_ports {AN[4]}]
set_property PACKAGE_PIN M17 [get_ports {AN[3]}]
set_property PACKAGE_PIN J14 [get_ports {AN[2]}]
set_property PACKAGE_PIN K13 [get_ports {AN[1]}]
set_property PACKAGE_PIN P14 [get_ports {AN[0]}]
set_property PACKAGE_PIN F14 [get_ports {seg[7]}]
set_property PACKAGE_PIN N14 [get_ports {seg[6]}]
set_property PACKAGE_PIN J13 [get_ports {seg[5]}]
set_property PACKAGE_PIN G13 [get_ports {seg[4]}]
set_property PACKAGE_PIN F13 [get_ports {seg[3]}]
set_property PACKAGE_PIN G14 [get_ports {seg[2]}]
```

```
set_property PACKAGE_PIN M13 [get_ports {seg[1]}]
set_property PACKAGE_PIN H14 [get_ports {seg[0]}]
set_property PACKAGE_PIN U18 [get_ports rst_n]
set_property PACKAGE_PIN U17 [get_ports clk_im]
set_property PACKAGE_PIN V5 [get_ports {SW[1]}]
set_property PACKAGE_PIN T4 [get_ports {SW[0]}]
set_property PACKAGE_PIN V6 [get_ports K]
set_property PACKAGE_PIN R15 [get_ports PC_Write]
set_property PACKAGE_PIN U16 [get_ports IR_Write]
set_property PULLDOWN true [get_ports clk_1M]
set_property PULLDOWN true [get_ports CLR]
set_property PULLDOWN true [get_ports IR_Write]
set_property PULLDOWN true [get_ports K]
set_property PULLDOWN true [get_ports PC_Write]
set_property PULLDOWN true [get_ports rst_n]
set_property PULLDOWN true [get_ports {SW[1]}]
set_property PULLDOWN true [get_ports {SW[0]}]
set_property PULLDOWN true [get_ports clk_im]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets clk_1M]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets clk_im]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets CLR]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets rst_n]
```

## 六、思考与探索

### 1、实验结果记录:

(实验操作的过程及结果记录)

PC	IR	COE 文件中指令代码	汇编指令	立即数 imm32	解析字段 是否正确
0000_000c	00a0_0393	00a00393	li t2,10	0000_000a	正确
0000_0014	0403_2e03	04032e03	lw t3,64(t1)	0000_0040	正确
0000_0030	09c0_2023	09c02023	sw t3,128(zero) #80<Loop2+0x5c>	0000_0080	正确
0000_0024	0003_8463	00038463	beq zt2,24<Loop2>	0000_0008	正确
0000_0018	01c2_82b3	01c282b3	add t0,t0,t3	0000_0000	正确
0000_001c	0043_0313	00430313	addi t1,t1,4	0000_0004	正确
0000_0028	fedf_f06f	fedff06f	j c <Loop1>	ffff_ffec	正确

### 2、实验结论:

实验结果符合预期结果, 逻辑正确, 实验成功。

### 3、问题与解决方案

编写译码块时测试时出现一直只出现 0 不变的情况, 无法分析出正确的立即数。考虑不周全, 忘了编写移位指令的逻辑, 编写后, 可以输出正常结果。

### 4、思考题:

1. 在复位后, 第一次按动 clk\_im 按钮, 你的程序读出的指令是哪个单元的? 0 号单元还是 4 号单元的指令? 分析为什么? 如果要求在复位后的第一个 clk\_im 来临时, 读出的是 0 号单元的指令, 你实现了吗? 如果没有实现, 尝试修改程序实现。(提示: 请关注 rst\_n 按键和 clk\_im 按键的有效边沿)

答: 在复位后, 第一次按动 clk\_im 按钮, 你的程序读出的指令是 0 号单元的。因为先读出所在单元的指令, PC 再进行+4 操作。实现了。

2. 你的实验能同时观察 PC 和 IR (即 inst) 的值吗? 如果可以, 请分析指令地址和指令代码是否匹配? 如果不匹配, 请分析原因。

答: 可以同时观察 PC 和 IR(inst)。指令地址和指令代码匹配。

3. 你在板级验证中, 每按一下 clk\_im 按键, 指令是否按序一条一条读出? PC 是否+4 或者只+4? 你是如何判断的? 分析为什么会出现不正常情况, 提出解决办法。

答: 是。看 PC 值是否在按下 clk\_im 按键+4. 无不正常情况。

4. 说说你在实验中碰到了哪些问题, 你是如何解决的?

答：编写译码块时测试时出现一直只出现 0 不变的情况，无法分析出正确的立即数。考虑不周全，忘了编写移位指令的逻辑，编写后，可以输出正常结果。