

# 实验报告

2021 年 5 月 16 日

成绩: \_\_\_\_\_

姓名	刘合	学号		班级	
专业	计算机科学与技术		课程名称	计算机组成原理课程设计	
任课老师		指导老师		机位号	
实验序号	4	实验名称	存储器设计		
实验时间	2021.5.16	实验地点		实验设备号	

## 一、实验目的与要求

### 1、实验目的:

1. 学习使用 Vivado 或者 ISE 开发工具的 Memory IP 核, 设计生成存储器模块的方法;
2. 学习存储器的结构及读写原理, 掌握存储器的设计方法。

### 2、实验要求:

1. 使用 Vivado 或者 ISE 工具, 按照上述步骤新建一个  $64 \times 32$  位的 Single Port RAM 并使用 COE 关联文件初始化其内容。
2. 新建一个存储器模块, 端口如图 11.18 所示; 引用上述的存储器 IP 核, 连接实例与存储器模块的端口。
3. 编写仿真激励代码, 进行仿真测试, 确保存储器模块读写逻辑功能正确。
4. 针对使用的实验板卡, 设计存储器模块的板级验证实验方案, 编写顶层测试模块。观察图 11.18, 输入的电平信号有 32 位写入数据、6 位地址信号和一个写信号, 无论哪种实验板卡, 输入设备资源都不够。图 11.36 给出一个简单的板级验证方案, 由两位开关选择指定的四个常数, 作为写入存储器的数据。请参考实验 2 中的板级验证设计方法, 自行修改设计。

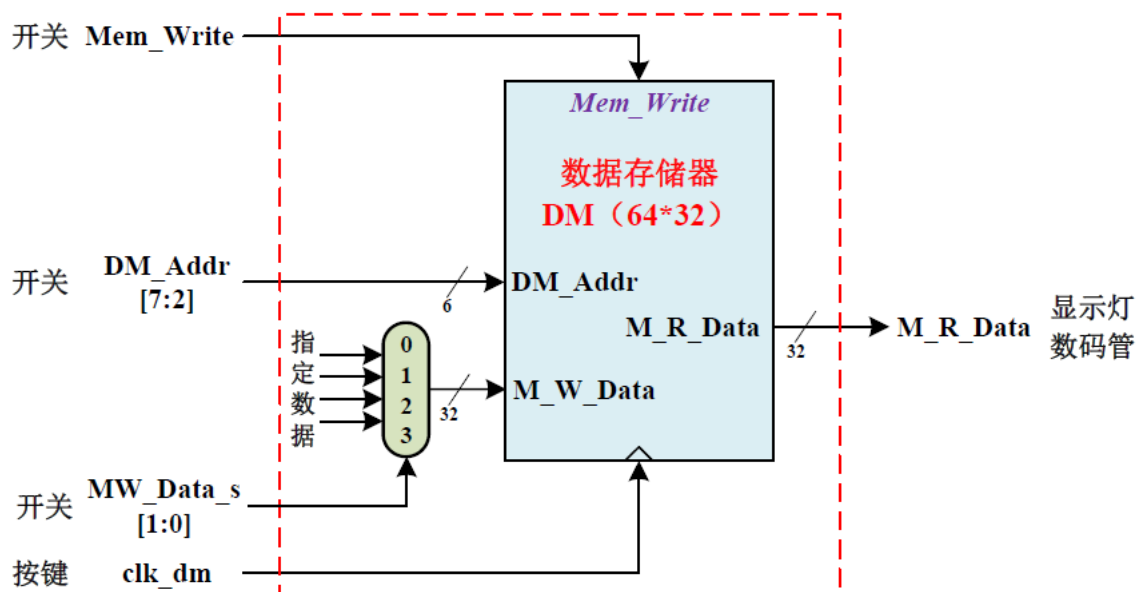


图11.36 实验4 顶层测试模块范例

5. 选择存储器单元地址，执行读写操作，验证你的存储器是否能正常存取，将实验结果记录到表中，要求存储器读和写功能都被有效测试。

6. 撰写实验报告，格式见附录，重点内容包括：对仿真结果进行分析；描述你设计的板级验证实验方案、模块结构与连接；说明你的板级操作过程；分析记录下来的板级实验结果、得到有效结论。请力所能及回答或实践本实验的“思考与探索”部分。

### 3. 实验步骤

1. 新建一个工程，通过 IP 核生成向导创建一个  $64 \times 32$  位的单端口 RAM IP 核，并创建与编辑一个 COE 文件，初始化该 RAM 的内容。

2. 新建一个存储器模块，输入输出端口如图 11.18 所示，其中引用上述生成的 RAM IP 核，并正确连接存储器模块端口与 IP 核实例的端口。

3. 编写激励代码，仿真验证存储器模块功能；分析仿真结果，确保读写操作正确。

4. 设计存储器模块板级验证的实验方案，然后据此编写一个顶层测试模块。

5. 可以依据实际需要，对顶层测试模块进行仿真测试，或者直接进入管脚约束环节。

6. 新建管脚约束文件，依据图 11.36 的提示及实际板卡情况，设计板级验证实验方案，进行相应的引脚配置。

7. 生成 \*.bit 文件，下载到实验设备的 FPGA 芯片中。

8. 板级实验：按照你所设计的实验方案，操作输入设备、观察输出设备，存储器读操作过程为：

- (1) 拨动开关输入存储器单元地址
- (2) 拨 Mem\_Write 开关 =0 按动 时钟键 clk\_dm
- (3) 观察输出设备上读出的存储器数据是否正确（与初始化数据一致，或者与最后一次写入的数据一致）

存储器写操作的过程为：

- (1) 拨动开关输入存储器地址；
- (2) 拨动开关，选择或者输入准备写入存储器的数据
- (3) 拨 Mem\_Write 开关 =1 按动时钟键 clk\_dm。

注意：在板级实验中, 要保证能观察或者经分析后确认：写入存储器的数据已经更新了指定存储器单元的值。分析实验结果是否正确

## 二、实验设计与程序代码

### 1、模块设计说明

程序包含了 4 个模块一个存储器 IP 核：

- 1.顶层模块：有序调用其他模块的程序；
- 2.分频器模块：是为了给数码管扫描显示模块分配时钟频率；
- 3.数码管扫描显示模块：是为了把 BCD 码数据以十进制数字显示出来
- 4.数据选择模块：选择不同的值存储到存储器。
5. 存储器 IP 核：存储数据

### 2.实验程序源代码及注释等

```
module chucun(CLR,clk_1M,clka,wea,addra,choice,AN,seg);//顶层模块
    input CLR;
    input clk_1M;
    input wire clka;
    input wire [0 : 0] wea;
    input wire [7 : 0] addra;
    input [2:0]choice;
    wire [31 : 0] dina;
    output [7:0]AN;
    output [7:0]seg;
```

```

wire CLK;

wire [31:0]douta;

xuanze ss(choice,dina);

RAM_B aa(
    .clka(clka),    // input wire clka
    .wea(wea),      // input wire [0 : 0] wea
    .addra(addra[7:2]), // input wire [5 : 0] addra
    .dina(dina),    // input wire [31 : 0] dina
    .douta(douta) // output wire [31 : 0] douta
);

fpq gg(CLR,clk_1M,CLK);

smgsm ff(CLK,CLR,douta,AN,seg);

endmodule

```

```

module xuanze(choice,dina);
    input [2:0]choice;
    output reg [31:0]dina;
    always@(*)
        begin
            case(choice)
                3'b000:dina=32'hffff_0f0f;
                3'b001:dina=32'h1111_1111;
                3'b010:dina=32'h2222_3333;
                3'b011:dina=32'habcd_3456;
                3'b100:dina=32'h2173_9803;
                3'b101:dina=32'hdadb_caca;
                3'b110:dina=32'h0000_0000;
                3'b111:dina=32'haaaa_bbbb;
            endcase
        end
end

```

```

endmodule

module fpq(CLR,clk_1M,CLK);          //分频器模块
    input CLR;
    input clk_1M;
    output reg CLK;
    reg [8:0]counter;
    always@(negedge CLR or posedge clk_1M)
        begin
            if(!CLR)
                begin
                    counter<=9'd0;
                    CLK<=1'b0;
                end
            else if(counter==9'd2000)
                begin
                    CLK<=~CLK;
                    counter<=9'd0;
                end
            else
                counter<=counter+1'b1;
            end
        end
endmodule

```

```

module smgsm(CLK,CLR,Choice,AN,seg);//数码管扫描显示模块
    input CLK; //扫描的间隔始终，控制数码管轮流点亮的频率
    input CLR; //复位信号，用于初始化状态
    input[31:0]Choice;
    output reg [7:0]AN;//位选
    output reg [7:0]seg; //段选
    reg [3:0] data;

```

reg [2:0] bit\_sel; //数码管计数器指示, 000~111 最左到最右

always@(negedge CLR or posedge CLK)

begin

if(!CLR)

bit\_sel<=3'b000;

else

bit\_sel<=bit\_sel+1'b1;

end

always@(\*)

begin

case(bit\_sel)

3'b000:data<=Choice[3:0];

3'b001:data<=Choice[7:4];

3'b010:data<=Choice[11:8];

3'b011:data<=Choice[15:12];

3'b100:data<=Choice[19:16];

3'b101:data<=Choice[23:20];

3'b110:data<=Choice[27:24];

3'b111:data<=Choice[31:28];

default:data<=data;

endcase

end

always@(\*)

begin

case(bit\_sel)

3'b000:AN=8'b11111110;

3'b001:AN=8'b11111101;

3'b010:AN=8'b11111011;

3'b011:AN=8'b11110111;

3'b100:AN=8'b11101111;

```

        3'b101:AN=8'b11011111;

        3'b110:AN=8'b10111111;

        3'b111:AN=8'b01111111;

        default:AN=8'b11111111;

    endcase

end

always@(*)
begin
    case(data)
        0:seg<=8'b00000011;

        1:seg<=8'b10011111;

        2:seg<=8'b00100101;

        3:seg<=8'b00001101;

        4:seg<=8'b10011001;

        5:seg<=8'b01001001;

        6:seg<=8'b01000001;

        7:seg<=8'b00011111;

        8:seg<=8'b00000001;

        9:seg<=8'b00001001;

        10:seg<=8'b00010001;

        11:seg<=8'b11000001;

        12:seg<=8'b01100011;

        13:seg<=8'b10000101;

        14:seg<=8'b01100001;

        15:seg<=8'b01110001;

        default:seg<=8'b11111111;

    endcase

end

endmodule

```

### 三、实验仿真

#### 1、 仿真代码

```
module ccqfz();

//INPUT

reg clka;

reg wea;

reg [5:0]addra;

reg [31:0]dina;

//OUTPUT

wire [31:0]douta;

initial

    begin

        clka=0;

        addra=6'b000000;

        forever #50 addra = addra + 1'b1;

    end

always

    begin

        #25 clka=~clka;

    end

/*initial

    begin

        #50 addra=5'b0000000;wea=0;dina=32'hFFFF_0F0F;

        #50 addra=5'b0000001;wea=0;dina=32'hFFFF_0F0F;

        #50 addra=5'b0000010;wea=0;dina=32'hFFFF_0F0F;

        #50 addra=5'b0000011;wea=0;dina=32'hFFFF_0F0F;

        #50 addra=5'b0000100;wea=0;dina=32'hFFFF_0F0F;

        #50 addra=5'b0000101;wea=0;dina=32'hFFFF_0F0F;
```



```

#50 addra=5'b000111;wea=0;dina=32'hFFFF_0F0F;

#50 addra=5'b000111;wea=1;dina=32'hFFFF_0F0F;

#50 addra=5'b000111;wea=0;dina=32'hFFFF_0F0F;

end*/

```

```


RAM_B vv(
    .clka(clka),    // input wire clka
    .wea(wea),      // input wire [0 : 0] wea
    .addra(addra),  // input wire [5 : 0] addra
    .dina(dina),    // input wire [31 : 0] dina
    .douta(douta)   // output wire [31 : 0] douta
);

endmodule

```

## 2、仿真波形


（运行仿真时，波形截图）

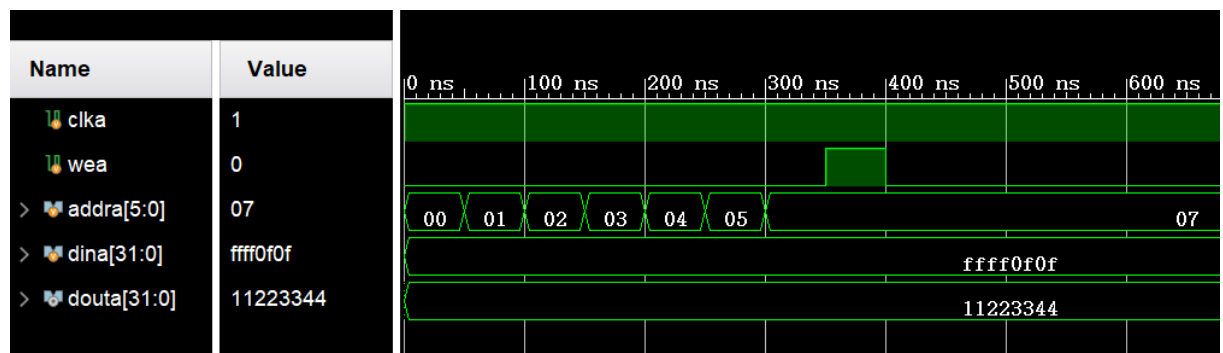

## 3、仿真结果分析

存储器读写功能都符合预期的效果。逻辑成功。

## 四、电路图

 

## 五、引脚配置

（引脚约束文件的内容，描述主要配置情况）

```
set_property IOSTANDARD LVCMOS18 [get_ports clka]
set_property IOSTANDARD LVCMOS18 [get_ports { addra[7]}]
set_property IOSTANDARD LVCMOS18 [get_ports { addra[6]}]
set_property IOSTANDARD LVCMOS18 [get_ports { addra[5]}]
set_property IOSTANDARD LVCMOS18 [get_ports { addra[4]}]
set_property IOSTANDARD LVCMOS18 [get_ports { addra[3]}]
set_property IOSTANDARD LVCMOS18 [get_ports { addra[2]}]
set_property IOSTANDARD LVCMOS18 [get_ports { choice[2]}]
set_property IOSTANDARD LVCMOS18 [get_ports { choice[1]}]
set_property IOSTANDARD LVCMOS18 [get_ports { choice[0]}]
set_property IOSTANDARD LVCMOS18 [get_ports { wea[0]}]
set_property IOSTANDARD LVCMOS18 [get_ports { AN[7]}]
set_property IOSTANDARD LVCMOS18 [get_ports { AN[6]}]
set_property IOSTANDARD LVCMOS18 [get_ports { AN[5]}]
set_property IOSTANDARD LVCMOS18 [get_ports { AN[4]}]
set_property IOSTANDARD LVCMOS18 [get_ports { AN[3]}]
set_property IOSTANDARD LVCMOS18 [get_ports { AN[2]}]
set_property IOSTANDARD LVCMOS18 [get_ports { AN[1]}]
set_property IOSTANDARD LVCMOS18 [get_ports { AN[0]}]
set_property IOSTANDARD LVCMOS18 [get_ports { seg[7]}]
set_property IOSTANDARD LVCMOS18 [get_ports { seg[6]}]
set_property IOSTANDARD LVCMOS18 [get_ports { seg[5]}]
set_property IOSTANDARD LVCMOS18 [get_ports { seg[4]}]
set_property IOSTANDARD LVCMOS18 [get_ports { seg[3]}]
set_property IOSTANDARD LVCMOS18 [get_ports { seg[2]}]
set_property IOSTANDARD LVCMOS18 [get_ports { seg[1]}]
set_property IOSTANDARD LVCMOS18 [get_ports { seg[0]}]
set_property IOSTANDARD LVCMOS18 [get_ports clk_1M]
set_property IOSTANDARD LVCMOS18 [get_ports CLR]
```

```
set_property PULLDOWN true [get_ports {addra[7]}]
set_property PULLDOWN true [get_ports {addra[6]}]
set_property PULLDOWN true [get_ports {addra[5]}]
set_property PULLDOWN true [get_ports {addra[4]}]
set_property PULLDOWN true [get_ports {addra[3]}]
set_property PULLDOWN true [get_ports {addra[2]}]
set_property PULLDOWN true [get_ports {choice[2]}]
set_property PULLDOWN true [get_ports {choice[1]}]
set_property PULLDOWN true [get_ports {choice[0]}]
set_property PULLDOWN true [get_ports {wea[0]}]
set_property PULLDOWN true [get_ports clk_1M]
set_property PULLDOWN true [get_ports CLR]
```

```
set_property PACKAGE_PIN E3 [get_ports clk_1M]
set_property PACKAGE_PIN U17 [get_ports CLR]
```

```
set_property PACKAGE_PIN F14 [get_ports {seg[7]}]
set_property PACKAGE_PIN N14 [get_ports {seg[6]}]
set_property PACKAGE_PIN J13 [get_ports {seg[5]}]
set_property PACKAGE_PIN G13 [get_ports {seg[4]}]
set_property PACKAGE_PIN F13 [get_ports {seg[3]}]
set_property PACKAGE_PIN G14 [get_ports {seg[2]}]
set_property PACKAGE_PIN M13 [get_ports {seg[1]}]
set_property PACKAGE_PIN H14 [get_ports {seg[0]}]
```

```
set_property PACKAGE_PIN C9 [get_ports {AN[7]}]
set_property PACKAGE_PIN C10 [get_ports {AN[6]}]
set_property PACKAGE_PIN D10 [get_ports {AN[5]}]
set_property PACKAGE_PIN C11 [get_ports {AN[4]}]
set_property PACKAGE_PIN M17 [get_ports {AN[3]}]
```

set\_property PACKAGE\_PIN J14 [get\_ports {AN[2]}]

set\_property PACKAGE\_PIN K13 [get\_ports {AN[1]}]

set\_property PACKAGE\_PIN P14 [get\_ports {AN[0]}]

set\_property PACKAGE\_PIN V5 [get\_ports {addra[7]}]

set\_property PACKAGE\_PIN T4 [get\_ports {addra[6]}]

set\_property PACKAGE\_PIN V6 [get\_ports {addra[5]}]

set\_property PACKAGE\_PIN T5 [get\_ports {addra[4]}]

set\_property PACKAGE\_PIN T6 [get\_ports {addra[3]}]

set\_property PACKAGE\_PIN V7 [get\_ports {addra[2]}]

set\_property PACKAGE\_PIN V15 [get\_ports {choice[2]}]

set\_property PACKAGE\_PIN R15 [get\_ports {choice[1]}]

set\_property PACKAGE\_PIN U16 [get\_ports {choice[0]}]

set\_property PACKAGE\_PIN V14 [get\_ports {wea[0]}]

set\_property PACKAGE\_PIN N17 [get\_ports clka]

set\_property CLOCK\_DEDICATED\_ROUTE FALSE [get\_nets clk\_1M]

set\_property CLOCK\_DEDICATED\_ROUTE FALSE [get\_nets clka]

set\_property CLOCK\_DEDICATED\_ROUTE FALSE [get\_nets CLR]

## 六、思考与探索

### 1、实验结果记录：

（实验操作的过程及结果记录）

存储器地址	初始化数据	读出数据	是否写入	写入新数据	读出数据
000000	1122_3344	1122_3344	否	FFFF_0F0F	1122_3344
000001	8899_aabb	8899_aabb	否	FFFF_0F0F	8899_aabb
000010	5555_6666	5555_6666	否	FFFF_0F0F	5555_6666

000011	2021_0303	2021_0303	否	FFFF_0F0F	2021_0303
000100	fff8_0f0f	fff8_0f0f	否	FFFF_0F0F	fff8_0f0f
000101	cabd_1234	cabd_1234	否	FFFF_0F0F	cabd_1234
000111	0000_0000	0000_0000	是	FFFF_0F0F	FFFF0F0F
000111	FFFF0F0F	FFFF0F0F	是	1111_1111	1111_1111

## 2、实验结论：

实验结果符合预期结果，逻辑正确，实验成功。

## 3、问题与解决方案：

在板级验证中，我需要按两次 clka 才能读出数据；

因为在 IP 核设置中勾选了“Primitives Output Register”选项，在第二个 clk 上跳沿才能读出数据。去掉勾选就解决了。

## 4、思考题：

1.) 在仿真测试和板级测试中，你是如何确认存储器单元被写入成功的？请具体说明。

**答：**先读取某个储存地址的内容，再写入数据到该存储地址，再次读取该存储地址的内容，如果已经变成了新写入的数据，则存储器单元被写入成功。

2.) 在板级实验中，你执行存储器写操作时，按下 clk\_dm 时钟键后，观察存储器读出的数据，是新写入的数据还是原来的数据？请你分析为什么会是这样的现象。

**答：**读出的数据是新写入的数据。写入数据速度快于读出数据。

3.) 接上题，请通过仿真测试，观察写操作的 clk\_dm 来临后，读出的数据是什么？和板级验证结果一致吗？分析原因。

**答：**不一致；在仿真中有延迟，先显示了写之前的数据，然后显示了写入后的数据。

6.) 谈谈你在实验中碰到了哪些问题？又是如何解决的？

**答：**在板级验证中，我需要按两次 clka 才能读出数据；因为在 IP 核设置中勾选了“Primitives Output Register”选项，在第二个 clk 上跳沿才能读出数据。去掉勾选就解决了。